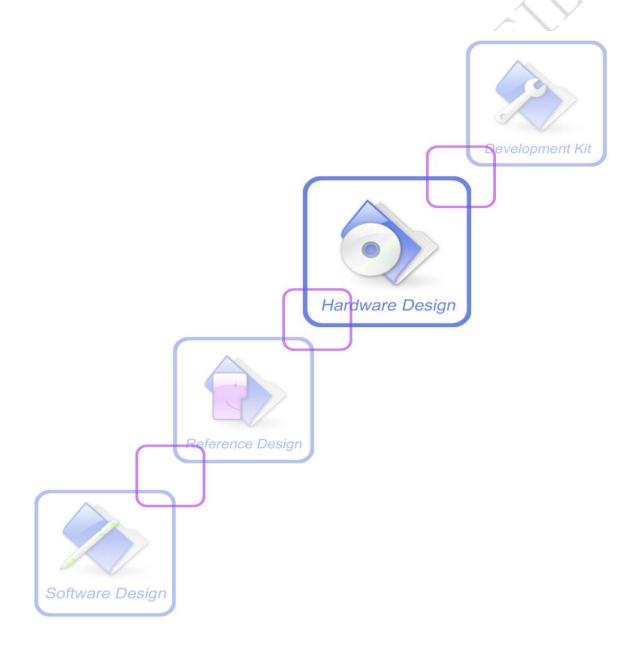




# Antenna Detecting Reference Design\_V1.01





| <b>Document Title</b>      | Antenna Detecting Reference Design       |  |  |  |
|----------------------------|--|--|--|--|
| Version                    | 1.01                                     |  |  |  |
| Date                       | 2012-01-10                               |  |  |  |
| Status:                    | Release                                  |  |  |  |
| <b>Document Control ID</b> | Antenna Detecting Reference Design_V1.01 |  |  |  |

#### **General Notes**

SIMCom offers this information as a service to its customers, to support application and engineering efforts that use the products designed by SIMCom. The information provided is based upon requirements specifically provided to SIMCom by the customers. SIMCom has not undertaken any independent search for additional relevant information, including any information that may be in the customer's possession. Furthermore, system validation of this product designed by SIMCom within a larger electronic system remains the responsibility of the customer or the customer's system integrator. All specifications supplied herein are subject to change.

#### Copyright

This document contains proprietary technical information which is the property of SIMCom Limited., copying of this document and giving it to others and the using or communication of the contents thereof, are forbidden without express authority. Offenders are liable to the payment of damages. All rights reserved in the event of grant of a patent or the registration of a utility model or design. All specification supplied herein are subject to change without notice at any time.

Copyright © SIMCom Wireless Solutions Co., Ltd, 2012



# **Contents**

| Version history |  |    |  |
|-----------------|--|----|--|
| 1 Int           | troductiontroduction                               | 5  |  |
| 2 Pa            | assive antenna supervisor                          | 5  |  |
| 2.1             | Passive antenna supervisor                         |    |  |
| 2.2             | Related AT Commands                                |    |  |
| 2.3             | Summary  |    |  |
| 3 Ac            | ctive antenna supervisor                           | 8  |  |
| 3.1             | Active antenna Introduction                        | 8  |  |
| 3.2             | Active antenna supervisor block diagram.           | 9  |  |
| 3.3             | Supervisor circuit.                                | 10 |  |
| 3.3             | 3.1 State diagram                                  | 11 |  |
| 3.4             | Related AT Commands                                |    |  |
| 3.5             | Status reporting.                                  | 13 |  |
| Figui           | re Index   |    |  |
| FIGUR           | RE 1: PASSIVE ANTENNA SUPERVISOR REFERENCE CIRCUIT | 5  |  |
| FIGUR           | RE 2: TYPICAL ACTIVE ANTENNA (EXTERNAL SUPPLY)     | 8  |  |
| FIGUR           | RE 3: TYPICAL ACTIVE ANTENNA (INTERNAL SUPPLY)     | 8  |  |
| FIGUR           | RE 4: FUNCTION BLOCK DIAGRAM                       | 9  |  |
| FIGUR           | RE 5: ACTIVE ANTENNA SUPERVISOR                    | 10 |  |
| FIGUR           | RE 6: LEVEL SHIFT FOR THE 1.8V ACTIVE ANTENNA      | 11 |  |
| FIGUR           | RE 7: STATE DIAGRAM OF ACTIVE ANTENNA SUPERVISOR   | 11 |  |
| Table           | e Index  |    |  |
| TABLE           | E 1: BOM OF PASSIVE ANTENNA SUPERVISOR CIRCUIT     | 6  |  |
| TABLE           | E 2: RELATED AT COMMANDS                           | 6  |  |
| TABLE           | E 3: URC REPORT FOR THE SUPERVISOR                 | 7  |  |
| TABLE           | E 4: GPIOS OF THE SUPERVISOR                       | 9  |  |
| TABLE           | E 5: BOM OF SUPERVISOR CIRCUIT                     | 10 |  |
| TABLE           | E 6: AT COMMANDS FOR ACTIVE ANTENNA SUPERVISOR     | 12 |  |
| TARIF           | F 7: RELATIONSHIP OF THE KEY PARAMETER             | 13 |  |



# **Version history**

| Date       | Version | Description of change         | Author       |
|------------|---------|-------------------------------|--------------|
| 2011-12-5  | 1.00    | Origin                        | Plato Chen   |
| 2012-01-10 | 1.01    | Add active antenna supervisor | Honggang .Ma |

# **SCOPE**

This document describes how to design antenna supervisor for SIMCom module, both the GSM antenna and GPS antenna are applied, care should be taken because active antenna is a little different for the LNA inside the antenna, so the AT commands and the detecting theory are also different.

Customers can also contact SIMCom FAE to confirm.

This document is subject to change without notice at any time.



# 1 Introduction

This document aims to support customers with antenna detecting design, for the different structure of passive and active antenna, the document mainly divided to two parts---passive antenna and active antenna.

Passive antenna is applied to GSM antenna and passive GPS antenna, the module must have ADC function and the antenna must be customized; Active GPS antenna is applied to active antenna supervisor, see following chapter for details.

# 2 Passive antenna supervisor

#### 2.1 Passive antenna supervisor

The following figure shows the reference circuit of passive antenna supervisor, it is also applied to GSM antenna, but the antenna must be customized, as the following figure shows, a resistance would be in serials between RF line and antenna ground.

For this circuit, the module must have ADC function to implement the function, and the software needs to be customized, customer can contact SIMCom FAE for details.

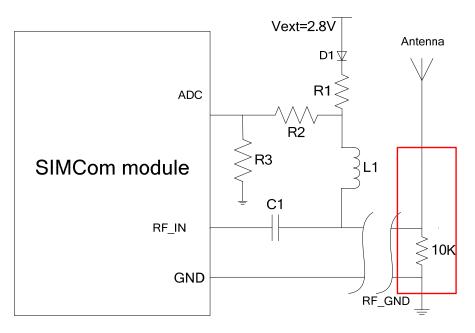


Figure 1: Passive antenna supervisor reference circuit



Table 1: BOM of passive antenna supervisor circuit

| References | Value     | Tolerance | Description            | Remarks |
|------------|-----------|-----------|------------------------|---------|
| R1,R2      | 15K       | ±1%       | Resistor, min 0.063 W  |         |
| R3         | 3.3K      | ±1%       |                        |         |
| D1         | RB060M-30 |           | Schottky barrier diode |         |
| L1         | 47nH      |           |                        |         |
| C1         | 33pF/50V  | ±5%       |                        |         |

(1) Pins introduction

ADC: Input Voltage range: 0-2.8V.

- (2) Antenna States:
  - ① Connected normally

The sampling voltage at ADC should be : 
$$V=(2.8-0.15)V^*\{ [ (R2+R3) //10K] \div [(R2+R3)//10K+R1] *R3 \div (R2+R3) = 2.65^* [6.466 \div (6.466 +15)] *3.3 \div 18.3 = 0.144V$$

2 Not connected

The sampling voltage at ADC should be : 
$$V=(2.8-0.15)V *[R3 \div (R1+R2+R3)]$$
  
=2.65\*(3.3 ÷ 33. 3)  
=0.263V

3 Connected to GND

The sampling voltage at ADC should be: V= 0V

4 Connected to other Power soUrce V<sub>O</sub>:

The sampling voltage at ADC should be V= 
$$V_0$$
 \*[R3÷(R2+R3)] =  $V_0$  \*(3.3÷18.3)

If  $V_0$  is 6V, then the  $V_{adc}$  is 1.082V, and  $V_{adc}$  is 2.164 when  $V_0$  is 12 V.

Note: This function needs to be supported by customized firmware.

#### 2.2 Related AT Commands

**Table 2: Related AT Commands** 

| AT+CANT Antenna Detecting |  |  |  |  |  |  |
|---------------------------|--|--|--|--|--|--|
| Test Command              | Response   |  |  |  |  |  |
| AT+CANT=?                 | +CANT: (list of supported <mode>s), (list of supported <urcenable>s),(list of supported</urcenable></mode> |  |  |  |  |  |
|                           | <timer>s)</timer>  |  |  |  |  |  |
|                           |  |  |  |  |  |  |
|                           | ОК   |  |  |  |  |  |
|                           | +CME ERROR: <err></err>  |  |  |  |  |  |



|   | Ginari madining dinari podicion  |  |  |  |  |
|---|--|--|--|--|--|
|   | Parameters   |  |  |  |  |
|   | See Write Command  |  |  |  |  |
| Read Command                              | Response   |  |  |  |  |
| AT+CANT?                                  | +CANT: <mode></mode>   | , <urce< th=""><th>nable&gt;, <timer></timer></th></urce<> | nable>, <timer></timer>                |  |  |
|   |  |  |  |  |  |
|   | ок   |  |  |  |  |
|   | +CME ERROR:  | <err></err>  |  |  |  |
|   | Parameters   |  |  |  |  |
|   |  |  |  |  |  |
|   | See Write Comman   | nd   |  |  |  |
| Write Command                             | Response   |  |  |  |  |
| AT+CANT=                                  | OK   |  |  |  |  |
| <mode>, [<urcenable>],</urcenable></mode> | +CME ERROR: <err></err>  |  |  |  |  |
| [ <urcenable>]</urcenable>                |  |  |  |  |  |
|   | Parameters   |  |  |  |  |
|   | <mode></mode>  | <u>0</u>   | Disable the antenna detecting function |  |  |
|   |  | 1  | Enable the antenna detecting function  |  |  |
|   |  |  |  |  |  |
|   | <ul><li><b>UrcEnable&gt;</b> <u>0</u> Disable reporting antenna state by URC</li></ul> |  |  |  |  |
|   | 1 Enable reporting antenna state by URC  |  |  |  |  |
|   |  |  |  |  |  |
|   | <ti>Reporting timer in units of seconds, range: 0—3600. Set timer to</ti>              |  |  |  |  |
|   | 0 will close detect, the recommend value is 10.  |  |  |  |  |
|   |  |  |  |  |  |

#### 2.3 Summary

**Table 3: Urc report for the supervisor** 

| ADC voltage (Unit: mV) | Antenna States                  | URC      |
|------------------------|---------------------------------|----------|
| < 15 (typical 7)       | Connected to GND                | +CANT:1  |
| 15-135                 | Connected to other power source | +CANT:2  |
| 135-160 (typical 144)  | Connected normally              | +CANT: 0 |
| 160-255                | Connected to other power source | +CANT:2  |
| 255-280 (typical 263)  | Not connected                   | +CANT:3  |
| > 280                  | Connected to other power source | +CANT:2  |

A design using a passive antenna requires more attention regarding the layout of the RF section. Typically a passive antenna is located near electronic components; therefore care should be taken to reduce electrical noise that may interfere with the antenna performance. Passive antennas do not require a DC bias voltage and can be directly connected to the RF input pin RF\_IN. Sometimes, they may also need a passive matching network to match the impedance to 50 Ohms.



# 3 Active antenna supervisor

#### 3.1 Active antenna Introduction

Active antenna has integrated with a low-noise amplifier (LNA). It can be directly connected to RF\_IN. If an active antenna is used, a proper supply should be fed to the pin VCC\_ANT, the pin VCC\_ANT has connected to the RF\_IN via a bead that used to separate the high frequency noise, Customers must pay attention to the supply of VCC\_ANT, clean and pure voltage is recommended. The power consumption of the active antenna is about 5 to 20mA, the following figure is the typical diagram of active antenna.

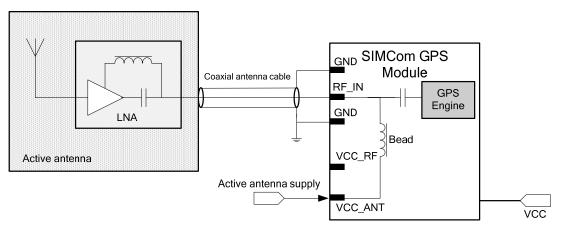


Figure 2: typical active antenna (external supply)

Usually, GPS modules from SIMCom have reserved a supply VCC\_RF for active antenna, customers can confirm the voltage in HD document, if the VCC\_RF match with the active antenna (see antenna datasheet to confirm), then the following diagram is the typical circuit.

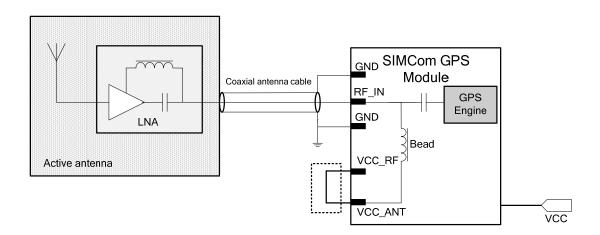


Figure 3: typical active antenna (internal supply)

Notes: this circuit doesn't support short-circuit protection, when the antenna shorted to GND, the supply can't be cut off.



#### 3.2 Active antenna supervisor block diagram

The supervisor circuit should detect and indicate all situations (short circuit, open circuit, normal connected), and when short circuit happens, the supply of the antenna should be turned off to protect GPS receiver. Especially, the supervisor can re-establish the active antenna when the wrong situation was corrected, every time a change appears, there will be an Urc reporting. The following figure is the block diagram of the supervisor circuit. (SIM900B and SIM18 are the typical module from SIMCom, sure other module applied to the supervisor also).

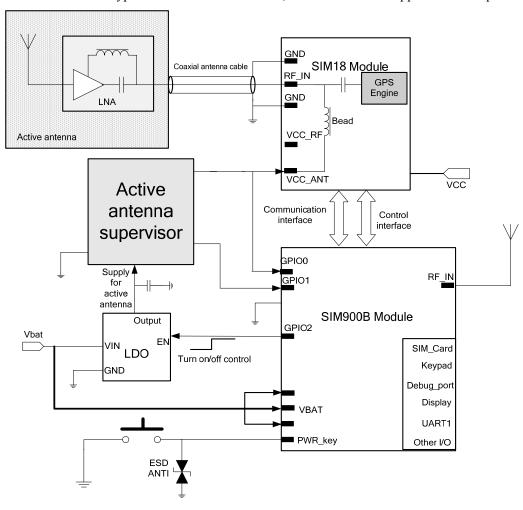


Figure 4: Function block diagram

Notes: the LDO output should match the active antenna. SIMCom suggest customers to use 3V active antenna. Sure 1.8V is also applied but the voltage level should be taken into consideration.

Table 4: GPIOs of the supervisor

| <b>GPIO</b> number in the Supervisor | GPIO in the SIM900B |            |  |  |
|--------------------------------------|---------------------|------------|--|--|
|                                      | Pin name            | Pin number |  |  |
| GPIO0                                | DISP_CLK            | 20         |  |  |
| GPIO1                                | DISP_CS             | 22         |  |  |
| GPIO2                                | DISP_DATA           | 18         |  |  |



When short circuit detected, the GPIO2 pin of SIM900B will pull down to shut down the LDO. And SIM900B will report the short happens by Urc (+CANT:0), and then SIM900B will pull up the GPIO2 to enable the supervisor circuit every 60 seconds to try to reestablish the active antenna circuit.

Notes: The recovery time can be set by AT Command provided by SIMCom, the default is 60s. See Table 5 for details.

#### 3.3 Supervisor circuit

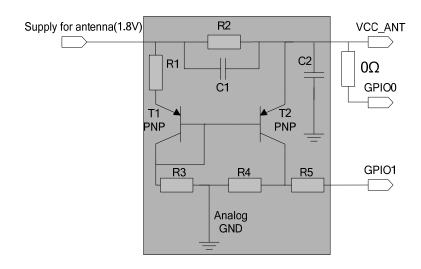


Figure 5: Active antenna supervisor

Table 5: BOM of supervisor circuit

| References | Value   | Tolerance Description |                          | Remarks                     |
|------------|---------|-----------------------|--------------------------|-----------------------------|
| C1         | 2.2 μF  | 10%                   | Capacitor, X7R, min 10 V |                             |
| C2         | 100 nF  | 10%                   | Capacitor, X7R, min 10 V |                             |
| R1         | 15 OHM  | 10%                   | Resistor, min 0.063 W    |                             |
| R2         | 10 OHM  | 10%                   | Resistor, min 0.250 W    |                             |
| R3, R4     | 10 KOHM | 10%                   | Resistor, min 0.063 W    |                             |
| R5         | 33 KOHM | 10%                   | Resistor, min 0.063 W    |                             |
| T1, T2     | PNP     |                       | PNP Transistor BC856B    | e.g. Philips Semiconductors |

GPIO0 and GPIO1 is the key of the supervisor circuit, SIM900B will judge the value of GPIO0 first, if the value is low which means that short circuit happens, the supervisor will be shut off immediately, and then trying to reestablish connection every 60 seconds.

If the value of GPIO0 is not low, then SIM900B will judge the status of GPIO1, for details please refer to table 7.



If the 1.8V active antenna is introduced, customer needs to shift the voltage to 2.8V so that the GPIO of SIM900B can realize the INT event. The following figure is the typical level shift circuit implemented by NPN transistor.

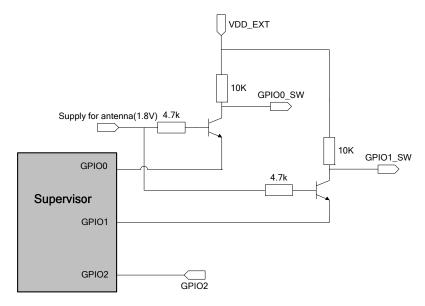


Figure 6: level shift for the 1.8V active antenna

#### 3.3.1 State diagram

The active antenna supervisor provides the methods to check the active antenna for open and short circuit, and to shut off the antenna supply if a short circuit detected. As the Figure 6 shows, if an antenna connected, the initial state after power-up is "Active Antenna OK".

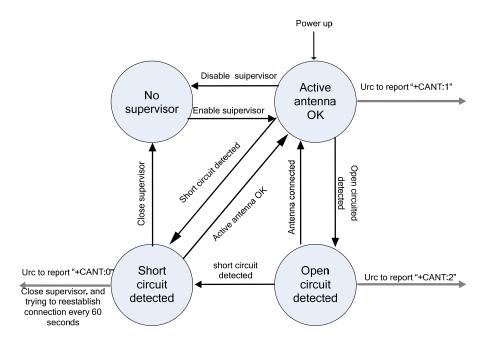


Figure 7: State diagram of active antenna supervisor



## 3.4 Related AT Commands

SIMCom module firmware supports an active antenna supervisor circuit, the default is closed, and customers need to active it by AT commands provided by SIMCom, as table 5 shows:

Table 6: AT Commands for active antenna supervisor

| AT+CANT Antenna I   | Detecting   |  |  |  |  |
|---|---|--|--|--|--|
| Test Command AT+CANT=?                                    | Response +CANT: (list of supported <enable>s, <timer>)  OK +CME ERROR: <err> Parameters</err></timer></enable>  |  |  |  |  |
| Read Command AT+CANT?                                     | See Write Command  Response +CANT: <enable>, <timer> OK +CME ERROR: <err></err></timer></enable>  |  |  |  |  |
|   | Parameters <enable> 0 Disable the antenna detecting function 1 Enable the antenna detecting function  <timer> 1-1000s can be set by user, the supervisor will try to reestablish the connection every <i>Timer</i> time when the short happened.</timer></enable> |  |  |  |  |
| Read Command AT+CANTSTATUS?                               | Response + CANTSTATUS: < Status> OK +CME ERROR: <err></err>   |  |  |  |  |
|   | Parameters <status>  0 The supply of the active antenna shorted to GND 1 The antenna equipped normally 2 Open circuit happens 3 unknown, the supervisor doesn't open</status>   |  |  |  |  |
| Write Command AT+CANT= <enable>, <timer></timer></enable> | Response  OK +CME ERROR: <err></err>  |  |  |  |  |
|   | Parameters <enable> 0 Disable the antenna detecting function 1 Enable the antenna detecting function  <timer> 1-1000s can be set by user, the supervisor will try to reestablish</timer></enable>   |  |  |  |  |
|   | the connection every <i>Timer</i> time after the short happened.  |  |  |  |  |



## 3.5 Status reporting

After SIM900B powered up, customers need to use AT commands to enable the supervisor circuit, then the supervisor circuit begins to work, and SIM900B will output messages to indicate the status of the active antenna every time the status got change.

As figure 4 shows, SIM900B watch the GPIO0 and GPIO1, the logic relationship as the following table shows:

**Table 7: Relationship of the key parameter** 

| item  | GPIO0 0 | GPIO1 | GPIO2     | Urc report | Status        |
|-------|---------|-------|-----------|------------|---------------|
| Value | 0       | /     | Pull down | +CANT: 0   | Short circuit |
|       | 1       | 1     | Keep up   | +CANT:2    | Open          |
|       | 1       | 0     | Keep up   | +CANT:1    | Normal        |



#### **Contact us:**

## Shanghai SIMCom wireless solutions Ltd.

Address: Building A, SIM Technology Building, No. 633 Jinzhong Road, Shanghai,

P. R. China 200335 Tel: +86 21 3252 3300 Fax: +86 21 3252 2030 URL: www.sim.com/wm